

**MCA-104: Computer System Architecture**  
**Master of Computer Applications**  
**Minor Exam**

**Max. Marks: 20**

**Time: 1 Hour**

1. Starting from an initial value for R 11011101, determine the sequence of binary value in R after a logical shift-left, followed by a circular shift-right, followed by a logical shift-right and an arithmetic shift-right. (2)
2. Using a decoder and external gates, design the combinational circuit defined by the following three Boolean functions: (3)  
$$F1 = x'y'z + xz'$$
$$F2 = x'yz' + xy'$$
$$F3 = xyz' + xy$$
3. Implement the following Boolean functions with a multiplexer: (4)  
$$F(w, x, y, z) = \sum(2, 3, 5, 6, 11, 14, 15)$$
4. Design a 2-bit count-down counter. This is a sequential circuit with two flip flops and one input x. When x=0, the state of the flip-flops does not change. When x=1, the state sequence is 11, 10, 01, 00, 11, and repeat. (5)  
(2\*3=6)
5. Answer the following questions:
  - a. Add 00011001 and 00010100 using BCD addition.
  - b. Represent decimal number 89.46 into floating point binary representation.
  - c. Perform arithmetic operation  $(-42) - (-13)$  in binary using signed-2's complement representation for negative numbers.